

## Uglyface

The Uglyface is a circuit designed by Tim Escobedo. It takes the input signal from your instrument, amplifies it with a 386-type amplifier IC, and uses this to retrigger a free-running oscillator made with a 555 counter IC. In addition, the input signal's envelope can sweep the frequency of the oscillator. The end result is a buzzsaw synthy distortion, capable of octave effects and faux-resonant filter sounds.

Designed by Tim Escobedo:

<http://folkurban.com/Site/GuitarEffects-681.html>

<http://www.jiggawoo.eclipse.co.uk/guitarhq/Circuitsnippets/snippets.html>

## Quantity - Part [notes]

### ICs

1 - JRC 386D

1 - ICM 7555

[other versions of the 555 and 386 can work if you want to experiment, but these part numbers are confirmed to work properly]

### Resistors

1 - 1m

1 - 1k

1 - 22k

1 - 470r

1 - 100k

1 - 4k7 [this resistor is the LED current limiting resistor - lower the value if using lower brightness LEDs, raise the value if the LED is too bright]

### Potentiometers

2 - A100K

1 - B1k

1 - B10k

### Capacitors

[capacitor dielectric types are just suggestions - if you want to use other types and you know what you're doing, feel free to experiment]

3 - 100N film

2 - 2.2uf electrolytic (AKA 2U2)

1 - 22uf electrolytic

### Optocoupler

1 - VTL5C3 [NSL-32 is also confirmed to work - other opto types can generally be used if they have a similar light/dark resistance spread - check the datasheet if unsure]


### Diodes


1 - 1n4001

1 - LED

Connect all together at the input jack ground

All pots shown from behind

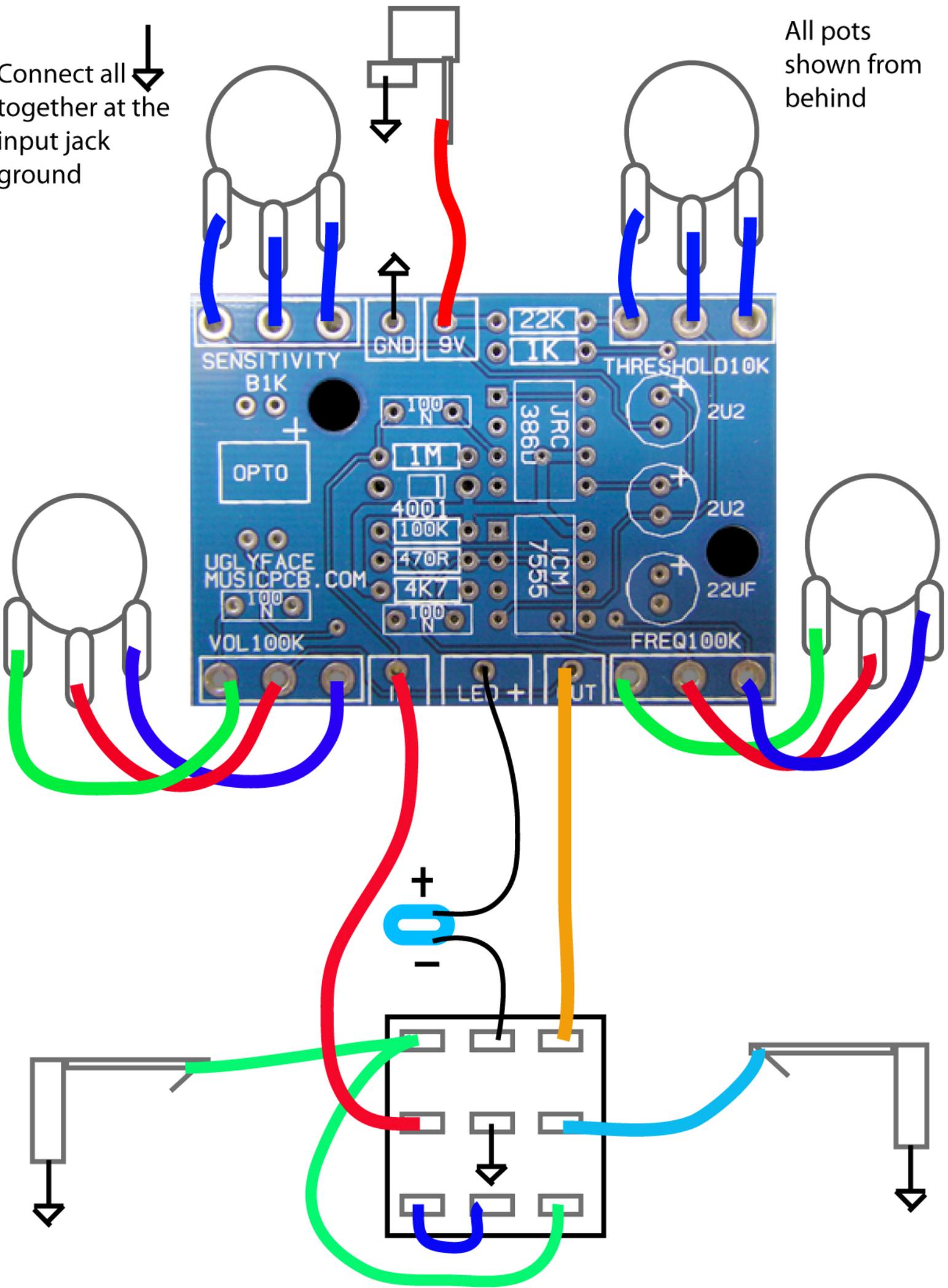

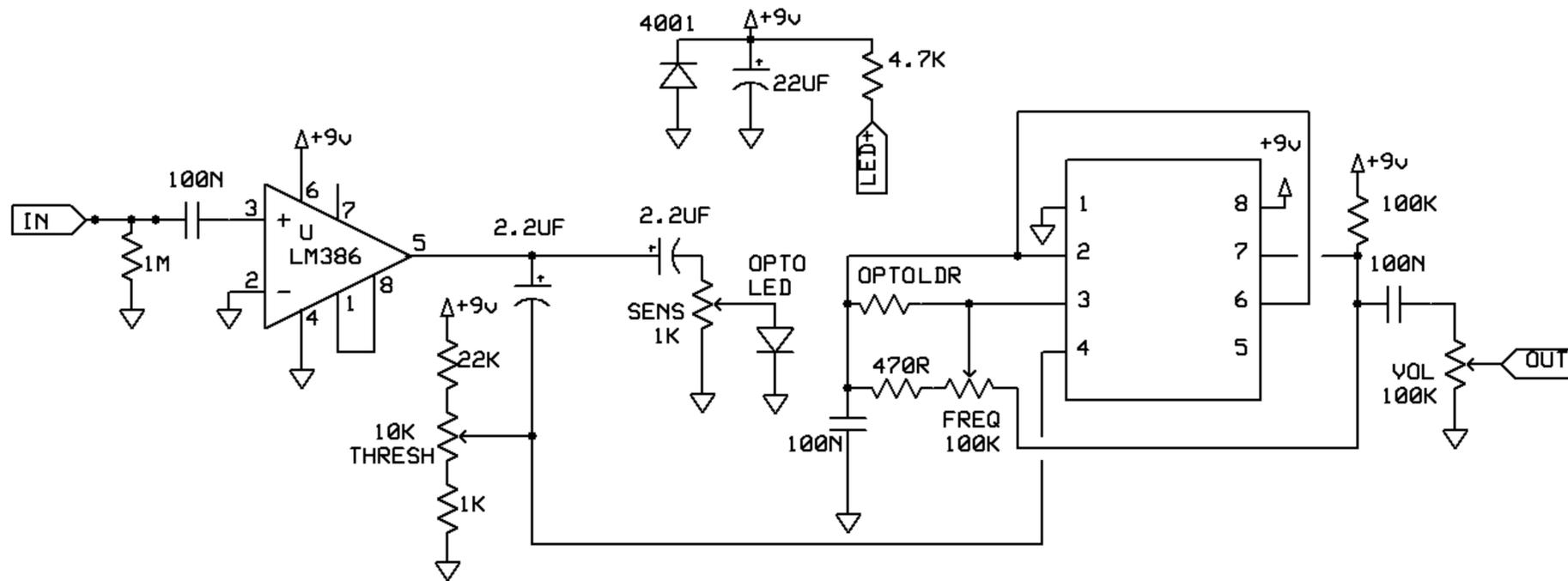

<b>Tim Escobedo</b>	
<b>Uglyface</b>	
Musicpcb.com	Rev 1.0
	11/24/2011